

DIGITAL ELECTRONICS (BCA 103)


**DEPARTMENT OF COMPUTER SCIENCE
PROGRAMME: BCA**



**CENTRAL UNIVERSITY OF ODISHA
KORAPUT**

SEQUENTIAL CIRCUIT

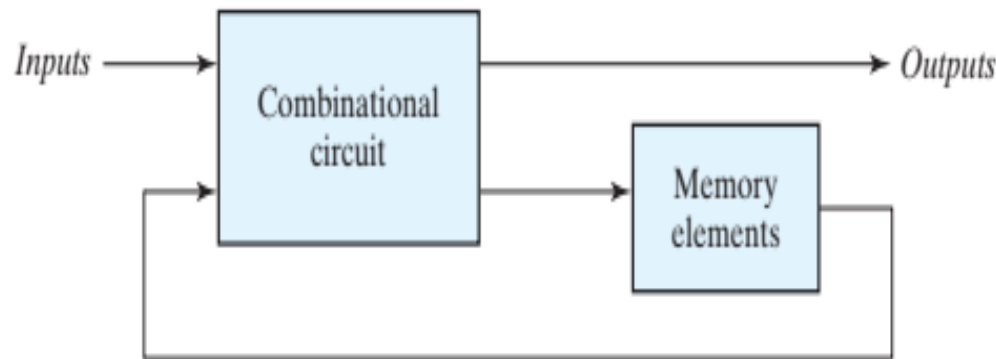- Combinational Circuit—their output depends only and immediately on their inputs—they have no memory, i.e., dependence on past values of their inputs.
- Sequential circuits, however, act as storage elements and have memory.
- They can store, retain, and then retrieve information when needed at a later time.



- The storage elements are devices capable of storing binary information.
- The binary information stored in these elements at any given time defines the *state* of the sequential circuit at that time.
- The sequential circuit receives binary information from external inputs that, together with the present state of the storage elements, determine the binary value of the outputs.
- These external inputs also determine the condition for changing the state in the storage elements.
- The next state of the storage elements is also a function of external inputs and the present state.
- Thus, a sequential circuit is specified by a time sequence of inputs, outputs, and internal states.

TYPES OF SEQUENTIAL CIRCUIT

- Based on **function of the timing signals**, sequential circuit are two types:
- i) Synchronous sequential circuit
- ii) Asynchronous sequential circuit

•

Synchronous

- The feedback to the input for next output generation is governed by clock signals.
- The memory unit which is being get used for governance is clocked flip flop.
- The states of Synchronous sequential circuits are always predictable and thus reliable.

Asynchronous

- Not governed by clock signals.
- Unclocked flip flop or time delay is used as memory element.
- There are chances for the Asynchronous circuits to enter into a wrong state because of the time difference between the arrivals of inputs. This is called as race condition.

Synchronous

- Output behaviour depends on the input at discrete time.
- Inputs and outputs are considered at discrete time instants.

Asynchronous

- Output behaviour depends on the sequence in which the input changes.
- Inputs and outputs signals are defined at every value of time.

Synchronous



- Easy to describe, analyze and design.
- Due to the propagation delay of clock signal in reaching all elements of the circuit the Synchronous sequential circuits are slower in its operation speed.
- Ex: counters, shift registers, memory units.

Asynchronous

- Difficult to describe, analyze and design.
- Since there is no clock signal delay, these are fast compared to the Synchronous Sequential Circuits.
- Ex: simple microprocessors, digital signal processing units and in communication systems for email applications, internet access and networking.

Synchronous Clocked Sequential Circuit

•

 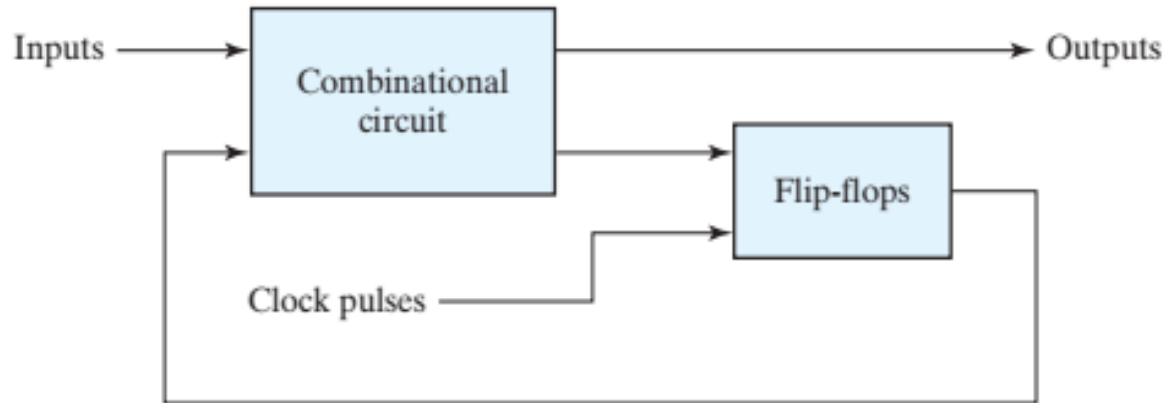


Timing diagram of clock pulses


- The storage elements (memory) used in clocked sequential circuits are called *flipflops*.
- A flip-flop is a binary storage device capable of storing one bit of information.
- In a stable state, the output of a flip-flop is either 0 or 1.
- A sequential circuit may use many flip-flops to store as many bits as necessary.
- The *outputs* are formed by a combinational logic function of the inputs to the circuit or the values stored in the flip-flops (or both).
- The value that is stored in a flip-flop when the clock pulse occurs is also determined by the inputs to the circuit or the values presently stored in the flip-flop (or both).
- The new value is stored (i.e., the flip-flop is updated) when a pulse of the clock signal occurs.



- Prior to the occurrence of the clock pulse, the combinational logic forming the next value of the flip-flop must have reached a stable value.
- If the clock (synchronizing) pulses arrive at a regular interval, the combinational logic must respond to a change in the state of the flip-flop in time to be updated before the next pulse arrives.
- Propagation delays play an important role in determining the minimum interval between clock pulses that will allow the circuit to operate correctly.
- A change in state of the flip-flops is initiated only by a clock pulse transition.

- A storage element in a digital circuit can maintain a binary state indefinitely (as long as power is delivered to the circuit), until directed by an input signal to switch states.
- The major differences among various types of storage elements are in the number of inputs they possess and in the manner in which the inputs affect the binary state.
- Storage elements that operate with signal levels (rather than signal transitions) are referred to as latches; those controlled by a clock transition are flip-flops.
- Latches are said to be level sensitive devices; flip-flops are edge-sensitive devices.

 


Definition of clock pulse transition

 

  


Triggers on this edge
of the clock pulse

 


Positive Edge Triggering

Triggers on this edge
of the clock pulse

 


Negative Edge Triggering

 

High Level Triggering

Triggers on low clock level

 

Low Level Triggering

Triggering

- **Triggering:** This means making a circuit active.
- Making a circuit active means allowing the circuit to take input and give output.
- There are basically two types of triggering.
- The triggering is given in form of a clock pulse or gating signal.
- Depending upon the type of triggering mechanism used, the circuit will become active at specific states of the clock pulse.
- **1. Level Triggering:** In the sequential circuit, if the output changes during the high voltage period or low voltage period, it is called level triggering.
- In level triggering the circuit will become active when the gating or clock pulse is on a particular level.
- This level is decided by the designer. We can have a negative level triggering in which the circuit is active when the clock signal is low or a positive level triggering in which the circuit is active when the clock signal is high.

- **2. Edge Triggering:** In a sequential circuit, if the output changes when the signal transits from a high level to a low level or from a low level to a high level, we call it edge triggering.
- In edge triggering the circuit becomes active at negative or positive edge of the clock signal.
- For example if the circuit is positive edge triggered, it will take input at exactly the time in which the clock signal goes from low to high.
- Similarly input is taken at exactly the time in which the clock signal goes from high to low in negative edge triggering.
- But keep in mind after the the input, it can be processed in all the time till the next input is taken.


Latch

- Latches are the basic circuits from which all flip-flops are constructed.
- Although latches are useful for storing binary information and for the design of asynchronous sequential circuits, they are not practical for use as storage elements in synchronous sequential circuits.

Flip-Flop


- A flip-flop circuit can maintain a binary state indefinitely(as long as power is deliver to the circuit) until directed by an input signal to switch states.
- The major differences among various types of flip-flops are in the number of inputs they possess and in the manner in which the inputs affect the binary state.
- A flip-flop can be constructed from two **NAND** gates or **NOR** gates.
- Each circuit forms a basic flip-flop upon which other more complicated types can be built.
- The cross-coupled connection from the output of one gate to the input of the other gate constitutes a feedback path.
- For this reason, the circuits are classified as asynchronous sequential circuits.
- Each flip-flop has **two outputs Q and Q'**, and **two inputs, Set(S) and Reset(R)**.
- This type of flip-flop is sometimes called **a direct-coupled RS flip-flop, or SR latch**.

SR Latch with NAND Gate

 


X	Y	NAND
0	0	1
0	1	1
1	0	1
1	1	0

S	R	Q	Q'	
0	0			
0	1	1	0	SET
1	0			
1	1			

 


X	Y	NAND
0	0	1
0	1	1
1	0	1
1	1	0

S	R	Q	Q'	
0	0			
0	1	1	0	SET
1	0			
1	1	1	0	HOLD

 


X	Y	NAND
0	0	1
0	1	1
1	0	1
1	1	0

S	R	Q	Q'	
0	0			
0	1	1	0	SET
1	0	0	1	RESET
1	1	1	0	HOLD After S=0, R=1

 

X	Y	NAND
0	0	1
0	1	1
1	0	1
1	1	0

S	R	Q	Q'	
0	0			
0	1	1	0	SET
1	0	0	1	RESET
1	1	1	0	HOLD After S=0, R=1
		0	1	HOLD After S=1, R=0

 


X	Y	NAND
0	0	1
0	1	1
1	0	1
1	1	0

S	R	Q	Q'	
0	0	1	1	Forbidden
0	1	1	0	SET
1	0	0	1	RESET
1	1	1	0	HOLD After S=0, R=1
		0	1	HOLD After S=1, R=0

- It operates with both inputs normally at 1, unless the state of the latch has to be changed.
- The application of 0 to the S input causes output Q to go to 1, putting the latch in the set state.
- When the S input goes back to 1, the circuit remains in the set state.
- After both inputs go back to 1, we are allowed to change the state of the latch by placing a 0 in the R input.
- This action causes the circuit to go to the reset state and stay there even after both inputs return to 1.
- The condition that is forbidden for the NAND latch is both inputs being equal to 0 at the same time, an input combination that should be avoided.

SR Latch with NOR Gate

X	Y	NOR
0	0	1
0	1	0
1	0	0
1	1	0

 

(a) Logic diagram

S	R	Q	Q'
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$)
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$)
1	1	0	0 (forbidden)

(b) Function table


SR Latch with NOR Gate

- The output of a NOR gate is 0 if any input is 1, and that the output is 1 only when all inputs are 0.
- As a starting point, assume that the set input is 1 and the reset input is 0.
- Since gate 2 has an input of 1, its output Q' must be 0, which puts both inputs of gate 1 at 0, so that output Q is 1.
- When the set input is returned to 0, the outputs remain the same, because output Q remains a 1, leaving one input of gate 2 at 1.
- That causes output Q' to stay at 0, which leaves both inputs of gate number 1 at 0, so that output Q is a 1.
- In the same manner, it is possible to show that a 1 in the reset input changes output Q to 0 and Q' to 1.
- When the reset input returns to 0, the output do not change.

SR Latch with NOR Gate

- When a 1 is applied to both the set and the reset input, both Q and Q' output go to 0.
- This condition violates the fact that output Q and Q' are complement of each other.
- A flip-flop has two useful states.
- When $Q=1$ and $Q'=0$, it is in the set state(or 1-state).
- When $Q=0$ and $Q'=1$, it is in the clear state(or 0-state).
- The outputs Q and Q' are complement of each other and are referred to as the normal and complement outputs, respectively.
- The binary state of the flip-flop is taken to be the value of the normal output.

 RS Flip-Flop / SR Latch With Control Unit



(a) Logic diagram

C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	Q = 0; Reset state
1	1	0	Q = 1; Set state
1	1	1	Undefined

(b) Function table

RS Flip-Flop / SR Latch With Control Unit

- It consists of a basic flip-flop circuit and two additional NAND gates.
- The pulse input acts as an enable signal for the other two inputs.
- The outputs of NAND gates 3 and 4 stay at the logic 1 level as long as the CP input remains at 0.
- This is the quiescent condition for the basic flip-flop.
- When the pulse input goes to 1, information from the S or R input is allowed to reach the output.
- The set state is reached with $S=1$, $R=0$, and $CP=1$.
- This causes the output of gate 3 to go to 0, the output of gate 4 to remain at 1, and the output of the flip-flop at Q to go to 1.
- To change to the reset state, the inputs must be $S=0$, $R=1$, and $CP=1$.


RS Flip-Flop / SR Latch With Control Unit

- In either case, when CP returns to 0, the circuit remains in its previous state.
- When CP=1 and both the S and R inputs are equal to 0, the state of the circuit does not change.
- An indeterminate condition occurs when CP=1 and both S and R are equal to 1.
- This condition places 0's in the outputs of gate 3 and 4 and 1's in both outputs Q and Q'.
- When the CP input goes back to 0 (when S and R are maintained at 1), it is not possible to determine the next state, as it depends on whether the output of gate 3 or gate 4 goes to 1 first.

RS Flip-Flop / SR Latch With Control Unit


- The characteristic table shows the operation of the flip-flop in tabular form.
- Q is an abbreviation of $Q(t)$ and stands for the binary state of the flip-flop before the application of a clock pulse, referred to as the present state.
- The S and R columns give the possible values of the inputs, and $Q(t+1)$ is the state of the flip-flop after the application of a single pulse, referred to as the next state.
- The CP input is not included in the characteristic table.
- The two indeterminate states are marked with don't care X's in the map, since they may result in either 1 or 0.
- However, the relation $SR=0$ must be included as part of the characteristics equation to specify that both S and R can not equal to 1 simultaneously.

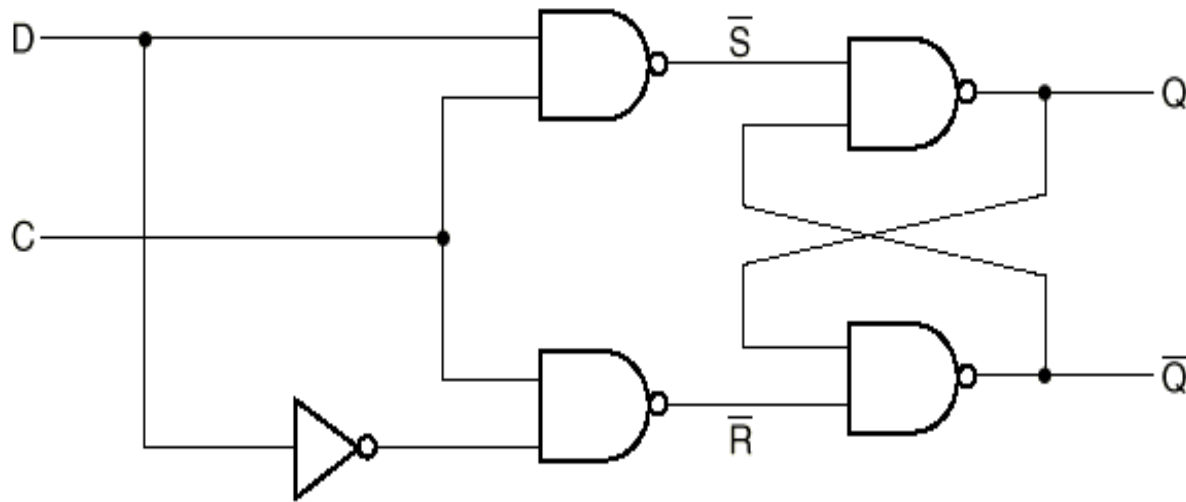D Latch (Transparent Latch) / D Flip-Flop



C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

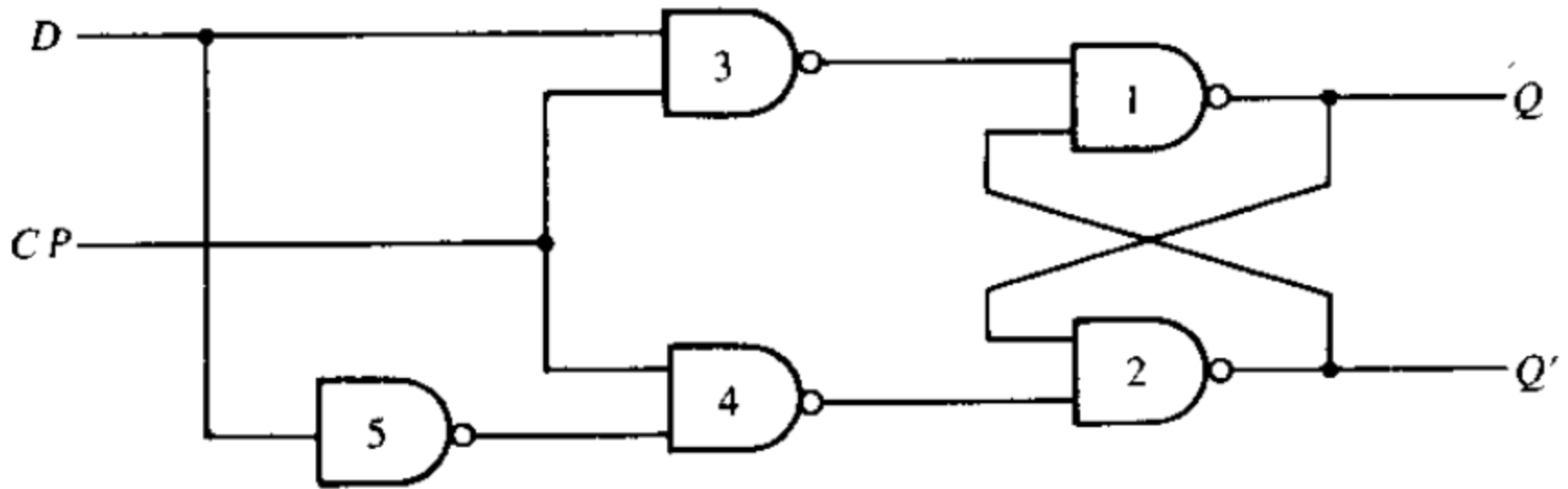D Latch (Transparent Latch) / D Flip-Flop



Q	D	$Q(t + 1)$
0	0	0
0	1	1
1	0	0
1	1	1


D Latch (Transparent Latch) / D Flip-Flop

- The undesirable condition of the indeterminate state in the RS flip-flop is that inputs S and R are equal to 1 at the same time.
- The D flip-flop has only two inputs: D and CP.
- The D input goes directly to S input and its complement is applied to the R input.
- As long as the pulse input is at 0, the outputs of gates 3 and 4 are at the 1 level and the circuit cannot change state regardless of the value of D.
- The D input is sampled when $CP=1$.
- If D is 1, the Q output goes to 1, placing the circuit in the set state.
- If D is 0, output Q goes to 0 and the circuit switches to the clear state.

D Latch (Transparent Latch) / D Flip-Flop

- The D flip-flop receives the designation from its ability to hold data into its internal storage.
- This type of flip-flop is sometimes called a gated D-latch.
- The CP input is often give the designation G(for gate) to indicate that this input enables the gated latch to make possible data entry into the circuit.
- The binary information present at the data input of the D flip-flop is transferred to the Q output when the CP input is enabled.
- The output follows the data input as long as the pulse remains in its 1 state.
- When the pulse goes to 0, the binary information that was present at the data input at the time the pulse transition occurred is retained at the Q output until the pulse input is enabled again.

JK Flip-Flop

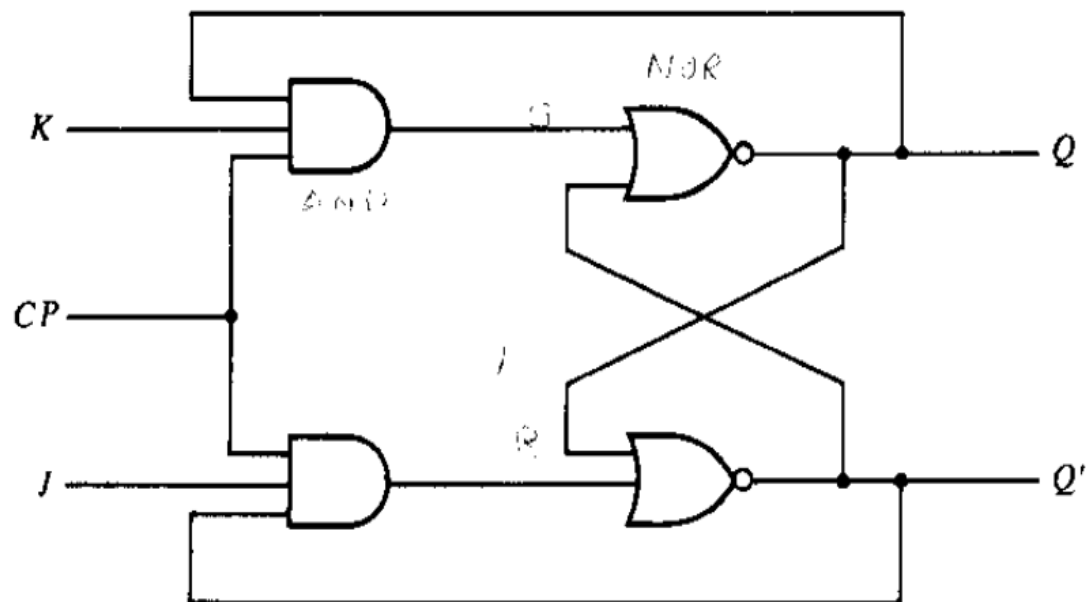

Q	J	K	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Q	JK		J	
	00	01	11	10
0			1	1
1	1			1

K

$$Q(t+1) = JQ' + K'Q$$

JK Flip-Flop

- A JK flip-flop is a refinement of the RS flip-flop in that the indeterminate state of the RS type is defined in the JK type.
- Inputs J and K behave like inputs S and R to set and clear the flip-flop, respectively.
- The input marked J is for set and the input marked K is for reset.
- When both inputs J and K are equal to 1, the flip-flop switches to its complement state, that is, if $Q=1$, it switches to $Q=0$, and vice versa.


JK Flip-Flop

- Output Q is ANDed with K and CP inputs so that the flip-flop is cleared during a clock pulse only if Q was previously 1.
- Similarly, output Q' is ANDed with J and CP inputs so that the flip-flop is set with a clock pulse only when Q' was previously 1.
- When both J and K are 1, the input pulse is transmitted through one AND gate only; the one whose input is connected to the flip-flop output that is presently equal to 1.
- Thus, if $Q=1$, the output of the upper AND gate becomes 1 upon application of the clock pulse, and the flip-flop is cleared.
- If $Q'=1$, the output of the lower AND gate becomes 1 and the flip-flop is set.
- In either case, the output state of the flip-flop is complemented.

JK Flip-Flop

- It is very important to realize that because of the feedback connection in the JK flip-flop, a CP pulse that remains in the 1 state while both J and K are equal to 1 will cause the output to complement again and repeat complementing until the pulse goes back to 0.
- To avoid this undesirable operation, the clock pulse must have a time duration that is shorter than the propagation delay time of the flip-flop.

T Flip-Flop

 

Q	T	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0


		T	
		0	1
Q	0		1
	1	1	

$$Q(t+1) = TQ' + T'Q$$

T Flip-Flop

- The T flip-flop is a single-input version of the JK flip-flop.
- The designation T comes from the ability of the flip-flop to “toggle”, or complement, its state.
- Regardless of the present state, the flip-flop complements its output when the clock pulse occurs while input T is 1.

Master-Slave Flip-Flop

 


Master-Slave Flip-Flop


- A master-slave flip-flop is constructed from two separate flip-flops.
- One circuit serves as a master and the other as a slave, and the overall circuit is referred to as a master-slave flip-flop.
- It consists of a master flip-flop, a slave flip-flop, and an inverter.
- When clock pulse CP is 0, the output of the inverter is 1.
- Since the clock input of the slave is 1, the flip-flop is enabled and output Q is equal to Y, while Q' is equal to Y'.
- The master flip-flop is disabled because CP=0.
- When the pulse becomes 1, the information then at the external R and S inputs is transmitted to the master flip-flop.
- The slave flip-flop, however, is isolated as long as the pulse is at its 1 level, because the output of the inverter is 0.
- When the pulse returns to 0, the master flip-flop is isolated, which prevents the external inputs from affecting it.
- The slave flip-flop then goes to the same state as the master flip-flop.

Constructing a Master-Slave D Flip-Flop From Two D Latches


Master

 

Slave

 

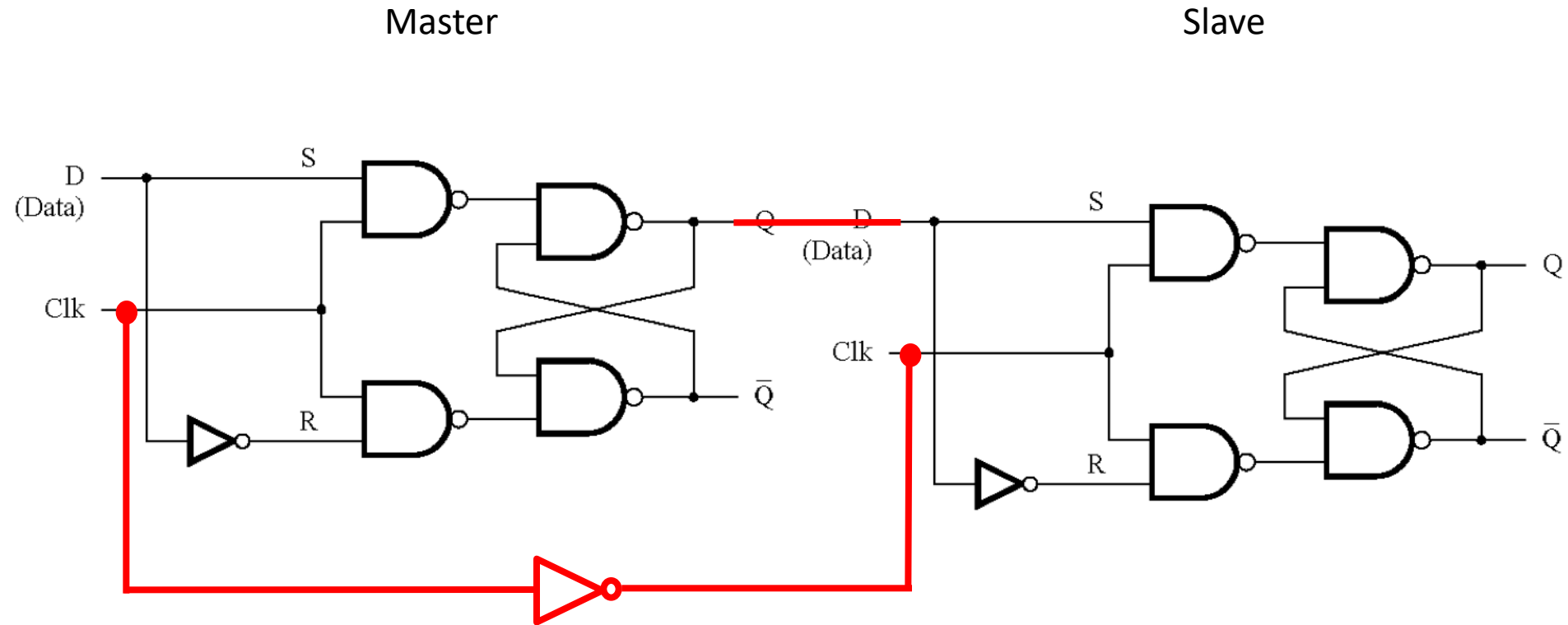
Constructing a Master-Slave D Flip-Flop From Two D Latches



Constructing a Master-Slave D Flip-Flop From Two D Latches

Master

Slave

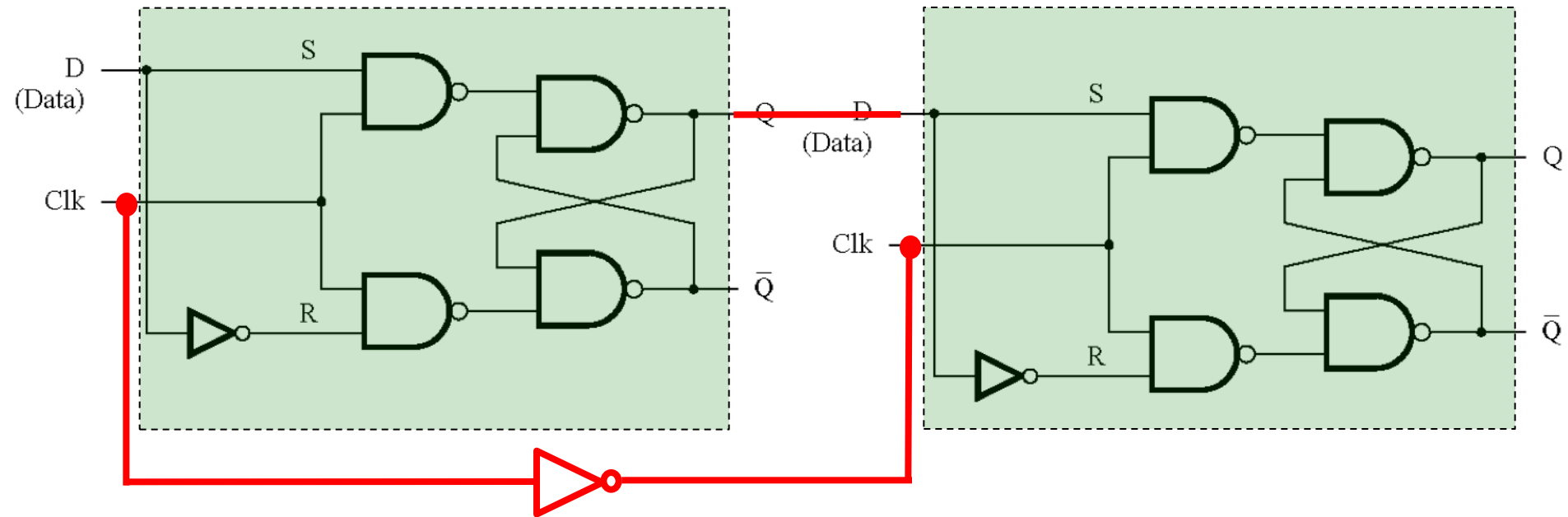

Constructing a Master-Slave D Flip-Flop From Two D Latches

